

Boolean Algebra

Why study Boolean Algebra?

It is highly desirable to find the simplest circuit implementation with the smallest number of gates or wires.

We can use *Boolean minimization* process to reduce a Boolean function (expression) to its simplest form: The result is an expression with the fewest literals and thus less wires in the final gate implementation.

Boolean Algebra (continued)

- George Boole (1815-1864), a mathematician introduced a systematic treatment of logic.
- He developed a consistent set of postulates that were sufficient to define a new type of algebra: Boolean Algebra (similar to Linear Algebra)
- Many of the rules are the same as the ones in Linear Algebra.

Laws of Boolean Algebra



- There are 6 fundamental laws, or axioms, used to formulate various algebraic structures:

1. *Closure*: Boolean algebra operates over a field of numbers, $B = \{0,1\}$:

For every x, y in B :

- $x + y$ is in B

- $x \cdot y$ is in B

  




Laws of Boolean Algebra (continued)

2. *Commutative* laws: For every x, y in B ,

- $x + y = y + x$

- $x \cdot y = y \cdot x$

» Similar to Linear Algebra

  
 


Laws of Boolean Algebra (continued)

3. *Associative laws*: For every x, y, z in B ,

- $(x + y) + z = x + (y + z) = x + y + z$
- $(xy)z = x(yz) = xyz$

» Similar to Linear Algebra

  

Laws of Boolean Algebra (continued)

4. *Distributive laws*: For every x, y, z in B ,

- $x + (y \cdot z) = (x + y)(x + z)$ [$+$ is distributive over \cdot]

» NOT Similar to Linear Algebra

- $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$ [\cdot is distributive over $+$]

» Similar to Linear Algebra

Laws of Boolean Algebra (continued)

5. Identity laws:

- A set B is said to have an identity element with respect to a binary operation $\{.\}$ on B if there exists an element designated by 1 in B with the property: $1 \cdot x = x$
Example: AND operation

- A set B is said to have an identity element with respect to a binary operation $\{+\}$ on B if there exists an element designated by 0 in B with the property: $0 + x = x$
Example: OR operation

» Similar to Linear Algebra

Laws of Boolean Algebra (continued)

6. Complement

For each x in B , there exists an element x' in B (the complement of x) such that:

- $x + x' = 1$
 - $x \cdot x' = 0$
- » Similar to Linear Algebra

We can also use \bar{x} to represent complement.

Laws of Boolean Algebra (Summary)

Commutative

$$x + y = y + x \quad xy = yx$$

Associative

$$(x + y) + z = x + (y + z)$$

$$(xy)z = x(yz)$$

Distributive

$$x + (yz) = (x + y)(x + z)$$

$$x(y + z) = (xy) + (xz)$$

Identity

$$x + 0 = x \quad x \cdot 1 = x$$

Complement

$$x + \bar{x} = 1 \quad x \cdot \bar{x} = 0$$

OR with 1 AND with 0

$$x + 1 = 1 \quad x \cdot 0 = 0$$

Other Theorems

▪ Theorem 1(a):

$$x + x = x$$

$$x + x = x$$

$$x + x = (x + x) \cdot 1$$

$$= (x + x)(x + x')$$

$$= xx + xx'$$

$$= x + 0$$

$$= x$$

▪ Theorem 1(b):

$$x \cdot x = x$$

$$x \cdot x = x$$

$$x \cdot x = xx + 0$$

$$= xx + xx'$$

$$= x(x + x')$$

$$= x \cdot 1$$

$$= x$$

Other Theorems (continued)

- Theorem 2(a):

$$x + 1 = 1$$

$$x + 1 = 1 \cdot (x + 1)$$

$$= (x + x')(x + 1)$$

$$= xx + x' \cdot 1$$

$$= x + x'$$

$$= 1$$

- Theorem 2(b):

$$x + xy = x$$

$$x + xy = x(1 + y)$$


$$= x(y + 1)$$

$$= x \cdot 1$$


$$= x$$

Gate Equivalency and DeMorgan's Law

$$x' \cdot y' = (x + y)'$$

 

$$x' + y' = (x \cdot y)'$$

 

Digital Logic Q's & A's


Q: Why is Gate Equivalency useful?

A: It allows us to build functions using only one gate type.


Q: Why are digital circuits constructed with NAND/NOR rather than with AND/OR?

A: NAND and NOR gates are smaller, faster, and easier to fabricate with electronic components. They are the basic gates used in all IC digital logic.

Digital IC's – Transistor Level

 


Digital IC's (continued)

 


Implementation of Boolean Functions

Example 1: $F_1 = x + y'z$

 

Implementation of Boolean Functions


Example 2: $F_1 = x'y'z + x'yz + xy'$

 

Implementation of Boolean Functions

- Try another implementation using a simplified F_2 :
 
$$\begin{aligned} F_2 &= x'y'z + x'yz + xy' \\ &= x'z(y'+y) + xy' \\ &= x'z(1) + xy' \\ &= x'z + xy' \end{aligned}$$




What are the advantages of this implementation?

This implementation has fewer gates and fewer inputs to the gates (or wires) than the previous one.

Simplifying Boolean Functions

- Simplify the following Boolean function to a minimum number of terms: $F_3 = xy + x'z + yz$
 
$$\begin{aligned}
 F_3 &= xy + x'z + yz \\
 &= xy + x'z + yz(x + x') \\
 &= xy + x'z + xyz + x'yz \\
 &= xy(1 + z) + x'z(1 + y) \\
 &= xy + x'z
 \end{aligned}$$




More on complements (DeMorgan)

- Find the complement of:
 $F = (AB' + C)D' + E$
 $F' = [(AB' + C)D' + E]'$
 $= [(AB' + C)D']' E'$
 $= [(AB' + C)' + D''] E'$
 $= [(AB')' C + D] E'$
 $= (A' + B)C' E' + DE'$
- Show that the complement of $x(x + y) = x'$
 $[x(x + y)]' = x' + (x + y)'$
 $= x' + x' y'$
 $= x'(1 + y')$
 $= x'(1) = x'$

Implementation of Boolean Functions

 
- Draw the logic diagram for the following function: $F = (a.b) + (b.c)$



Implementation of Boolean Functions

- Using ONLY NAND gates, draw a schematic for the following function: $F = (a.b) + (b.c)$

 
$$\begin{aligned}(F') &= [(a.b) + (b.c)]' \\ &= [(a.b)' . (b.c)']\end{aligned}$$



Implementation of Boolean Functions

- Using only OR and NOT gates, draw a schematic for the following function: $F = xy + x'y' + y'z$
 
$$\begin{aligned}(F') &= ((xy + x'y' + y'z)')' \\ &= [(xy)' \cdot (x'y')' \cdot (y'z)']' \\ &= [(x'+y') \cdot (x+y) \cdot (y+z)']' \\ &= (x'+y') + (x+y) + (y+z)'\end{aligned}$$



Minterms and Maxterms

- MINTERMS AND MAXTERMS:

n binary variables can be combined to form 2^n terms (AND terms), called minterms (SOP).

In a similar fashion, n binary variables can be combined to form 2^n terms (OR terms), called maxterms (POS).

* Note that each maxterm is the complement of its corresponding minterm and vice versa.

Minterms and Maxterms (continued)

Table 2-3:
Minterms and Maxterms for Three Binary Variables

x	y	z	minterms		Maxterms	
0	0	0	$x'y'z'$	m_0	$x+y+z$	M_0
0	0	1	$x'y'z$	m_1	$x+y+z'$	M_1
0	1	0	$x'yz'$	m_2	$x+y'+z$	M_2
0	1	1	$x'yz$	m_3	$x+y'+z'$	M_3
1	0	0	$xy'z'$	m_4	$x'+y+z$	M_4
1	0	1	$xy'z$	m_5	$x'+y+z'$	M_5
1	1	0	xyz'	m_6	$x'+y'+z$	M_6
1	1	1	xyz	m_7	$x'+y'+z'$	M_7

Sminterms and Pmaxterms

- Given the truth table, express F_1 in sum of minterms

x	y	z	F_1	F_2
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$F_1(x, y, z) = \sum(1,4,5,6,7) = m_1 + m_4 + m_5 + m_6 + m_7$$

$$= (x'y'z) + (xy'z') + (xy'z) + (xyz') + (xyz)$$

- Find F_2

Sminterms and Pmaxterms

- Repeat for product of maxterms.

x	y	z	F_1	F_2
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$F_1(x, y, z) = \prod(0,2,3) = M_0 \cdot M_2 \cdot M_3$$

$$= (x + y + z)(x + y' + z)(x + y' + z')$$

Sminterms and Pmaxterms

Express the Boolean function $F = x + y'z$ in a sum of minterms, and then in a product of Maxterms.

$$x = x(y + y') = xy + xy'$$

$$xy = xy(z + z') = xyz + xyz'$$

$$xy' = xy'(z + z') = xy'z + xy'z'$$

$$y'z = y'z(x + x') = xy'z + x'y'z$$

Adding all terms and excluding recurring terms:

$$F(x, y, z) = x'y'z + xy'z' + xy'z + xyz' + xyz \quad (\text{SOP})$$



$$F(x, y, z) = m_1 + m_4 + m_5 + m_6 + m_7 = \sum(1,4,5,6,7)$$

Product of maxterms (POS)? $\prod(0,2,3) = M_0 \cdot M_2 \cdot M_3$

XOR Logic gate

3-input exclusive-OR (XOR) logic gate:

$$F = X \oplus Y \oplus Z$$

  

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1